

11.13 Top-down design + examples

i This section has been set as optional by your instructor.

Top-down design: Capture, convert

Designers commonly follow a two-step design process:

1. **Capture**: The task of precisely describing a circuit's desired behavior.
2. **Convert** (aka **implement**): The task of translating captured behavior into a circuit, possibly involving simplification.

Capture: For combinational circuits, designers commonly capture behavior as truth tables or equations.

Convert: A truth table can be converted to an equation first by ORing the minterms of each table row having an output 1. An equation can be converted to a circuit by multiplying out to product terms (if not already), with each term becoming an AND gate, followed by one OR gate.

PARTICIPATION ACTIVITY 11.13.1: Top-down design: Capture, convert.

Consider a designer who wishes to design a circuit. Order the steps.

Convert: Truth table to equation

Capture as truth table

Convert: Equation to circuit

Use the circuit

(A)

(B)

(C)

(D)

Reset

Example: Medical radiation therapy device

A particular medical device delivers radiation to a patient to treat cancer. The device has two radiation strength levels, low ($s = 0$) and high ($s = 1$). The device has two radiation durations: short ($d = 0$) and long ($d = 1$). The device normally is used to deliver high strength for short duration, or low strength for long duration. A hardware safety component can be enabled ($e = 1$) that detects high strength for long duration and automatically turns off the device after a minute, but on rare occasion a radiation therapist may disable that component. To prevent accidents, a designer wishes to sound an alarm if the device is ever configured to high strength for long duration with the safety off.

PARTICIPATION ACTIVITY 11.13.2: Medical radiation therapy device: Warning system.

Start ☐ 2x speed

Control panel

Radiation delivery device

s

d


e

Warning system

Alarm

Capture $y = sde'$

Convert



PARTICIPATION ACTIVITY 11.13.3: Radiation delivery device.

Consider the radiation delivery device above.

1) For the warning system, how many inputs exist?

Check [Show answer](#)

2) A truth table would have had how many rows?

Check Show answer

- 3) The designer captured the desired behavior using what equation?

Check Show answer

- 4) The equation converted to how many AND and OR gates total?

Check Show answer

Exploring further:

- **Therac-25**: A well-known radiation therapy device with a bug that caused patient injury/death. (Source: Wikipedia)


Example: Weight threshold

A car's seat weight sensor provides three values a, b, c, to a system, indicating an object's relative weight in binary, ranging from 000 to 111 (heaviest). A designer wishes to design a "weight threshold" system that activates an airbag system ($y = 1$) if the weight is 101 (5) or more. For this system, the designer chooses to capture desired behavior with a truth table, then converts to a circuit.

PARTICIPATION ACTIVITY

11.13.4: Weight threshold system.

Start ☐ 2x speed

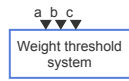


Capture

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Convert

$$y = ab'c + abc' + abc$$

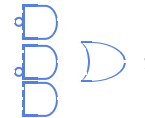

PARTICIPATION ACTIVITY

11.13.5: Weight threshold system.

Consider the weight threshold system above.

- 1) To capture the system's behavior, the designer used ____ .
☐ a truth table
☐ an equation
- 2) To convert the captured behavior to a circuit, the designer first ____ .
☐ simplified
☐ converted to an equation
- 3) To continue converting, the designer converted an equation to ____ .
☐ gates
☐ a truth table


Example: Majority voter circuit

Some systems are more prone to errors due to complexity or noise. And, some systems cannot tolerate errors. Ex: Spacecraft have complex control systems, are prone to errors due to noise/vibrations/heat, and may crash or explode if digital circuit outputs are erroneous. Such systems often have three independent calculations of output, and then use a circuit to take a majority vote, an arrangement known as *triple modular redundancy*.

PARTICIPATION ACTIVITY

11.13.6: Majority voter circuit.

Start ☐ 2x speed

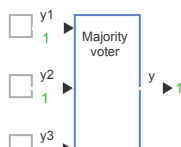

Capture

y1	y2	y3	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	1	1

Convert

$$y = y1y2y3 + y1y2y3' + y1y2'y3 + y1y2'y3'$$





0

1 1 0 1
1 1 1 1

DD

U

**PARTICIPATION
ACTIVITY**

11.13.7: Majority voter circuit.



Consider the example above.

- 1) The gray boxes on the left each ____ .
 - ☐ are majority voter circuits
 - ☐ carry out different functions
 - ☐ carry out the same function
- 2) The majority voter circuit has three inputs. What other number of inputs would be most reasonable?
 - ☐ One
 - ☐ Five
 - ☐ Twenty nine
- 3) If the inputs to the majority voter circuit are 1 0 1, the output should be ____ .
 - ☐ 0
 - ☐ 1
 - ☐ Error
- 4) The inputs to the voter circuit are ____ .
 - ☐ always the same
 - ☐ always different
 - ☐ usually the same
- 5) The voter circuit ____ correct output.
 - ☐ helps yield
 - ☐ guarantees



Exploring further:

- [Triple modular redundancy](#) (Source: Wikipedia)

 [Provide feedback on this section](#)