


12.7 NAND / NOR (universal gates)

NAND

A **NAND** gate is the opposite (the NOT, hence the "N") of an AND gate, outputting 0 if all inputs are 1s; else the output is 1.

Figure 12.7.1: NAND truth table and gate.

a	b	f
0	0	1
0	1	1
1	0	1
1	1	0

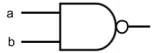

PARTICIPATION ACTIVITY

12.7.1: NAND gates.

1) 0 NAND 1 = ?

- ☐ 1
☐ 0

2) 1 NAND 1 = ?

- ☐ 1
☐ 0

3) 0 NAND 0 = ?

- ☐ 1
☐ 0

A NAND gate is a universal gate




NAND gates are popular due to having a simpler CMOS transistor circuit implementation than AND gates: Recall that an AND gate is built from a NAND transistor circuit followed by a NOT circuit.

Furthermore, NAND gates are popular due to being a universal gate. A **universal gate** is a single gate type that can implement any combinational circuit. NAND can implement NOT, AND, and OR, as shown below, and is thus universal.

PARTICIPATION ACTIVITY

12.7.2: NAND is a universal gate.

Start ☐ 2x speed

   

NAND is thus a universal gate

PARTICIPATION ACTIVITY

12.7.3: Universal gates.

1) A NAND gate is a universal gate.

- ☐ True
☐ False

2) A NAND gate cannot implement a NOT gate.

- ☐ True
☐ False

3) Inverting the output of a NAND gate produces an AND gate.

- ☐ True
☐ False

4) Inverting the inputs of a NAND gate

produces an OR gate.

- ☐ True
☐ False

Converting to NAND gates

NAND being a universal gate enables chip makers to pre-fabricate a chip consisting of millions of NAND gates. Any circuit of NAND gates can be implemented simply by adding wires. Pre-fabricating the chip with AND, OR, and NOT gates would involve complexities like deciding how many of each gate to pre-fabricate, and where to place each gate type. Using NAND is much simpler.

A chip with pre-fabricated gates is sometimes called a **gate-array ASIC**. **ASIC** is short for Application-Specific Integrated Circuit.




Converting an AND/OR/NOT circuit to a NAND-only circuit enables implementation using fewer transistors as well as enables implementation on a gate-array ASIC. The conversion can be done simply by replacing each AND, OR, and NOT gate by the equivalent structure of NAND gates, then removing double-inversions.

PARTICIPATION ACTIVITY

12.7.4: Converting to a NAND-only implementation.


Start ☐ 2x speed

$$q = a'b + cd$$

   

PARTICIPATION ACTIVITY

12.7.5: Converting to NAND gates.

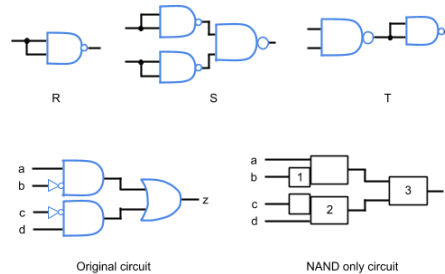

Consider the figure above. Which NAND pattern goes into which box?

1) Box 1

Check [Show answer](#)

2) Box 2


Check [Show answer](#)

3) Box 3

Check [Show answer](#)

PARTICIPATION ACTIVITY

12.7.6: Simplifying NAND circuits.

 

1) Which pair of NAND gates can be eliminated?

- ☐ 1, 2
☐

- ☐ 3, 4
☐ 4, 5

NOR

A **NOR** gate is the opposite of an OR gate, outputting 0 if any of the inputs are 1s; else the output is 1.

A discussion analogous to the above NAND discussion exists for NOR. Such discussion is omitted here. Briefly, NOR's transistor structure is simpler than OR's. NOR is also a universal gate. NOT: $(a + a)' = a'a' = a'$ (NOR with inputs tied together). OR: $((a + b))' = (a + b)' = a + b$ (NOR followed by NOT). AND: $(a' + b')' = a'b' = ab$ (NOR with each input NOTed).

Figure 12.7.2: NOR truth table and gate.

a	b	f
0	0	1
0	1	0
1	0	0
1	1	0



PARTICIPATION ACTIVITY

12.7.7: NOR gates.

- 1) $0 \text{ NOR } 0 = ?$

☐ 1
☐ 0
- 2) $1 \text{ NOR } 1 = ?$

☐ 1
☐ 0
- 3) $0 \text{ NOR } 1 \text{ NOR } 1 = ?$

☐ 1
☐ 0
- 4) A NOR gate is a universal gate.

☐ True
☐ False
- 5) An AND gate is a universal gate.

☐ True
☐ False
- 6) A NOT gate is a universal gate.

☐ True
☐ False

[Provide feedback on this section](#)