

# 12.9 Decoders

## Basics

A **decoder** is a combinational circuit that converts N inputs to a 1 on one of  $2^N$  outputs. A **2x4 decoder**, spoken as "2 to 4 decoder", converts two inputs to a 1 on exactly one of four outputs.

PARTICIPATION  
ACTIVITY

12.9.1: A 2x4 decoder.

Start ☐ 2x speed

1

i1

y3

1

i0

y2

y1

y0

i1	i0	y3	y2	y1	y0
1	0	0	0	0	1
0	1	0	0	1	0
0	0	1	0	1	0
1	1	1	0	0	0

PARTICIPATION  
ACTIVITY

12.9.2: 2x4 decoder.

Consider a 2x4 decoder.

1) If i1i0 = 00, then y1 = \_\_\_\_ .

Check [Show answer](#)

2) If i1i0 = 01, then y1 = \_\_\_\_ .

Check [Show answer](#)

3) i1i0 = \_\_\_\_ configures the decoder to output y0 = 0, y1 = 0, y2 = 0, and y3 = 1.

Check [Show answer](#)

4) How many outputs are set to 1 at any given time?  
Type: 0, 1, 2, 3, or 4

Check [Show answer](#)

5) i1i0 = \_\_\_\_ configures the decoder to output y0 = 0, y1 = 0, y2 = 1, and y3 = 1.  
Type: 00, 01, 10, 11, or \*\* if not possible.

Check [Show answer](#)

## Example: Lawn sprinkler controller

A lawn sprinkler system may have multiple zones. A sprinkler controller activates only one zone at a time, due to limited incoming water. The brain of the controller, typically a small computer, may encode the active zone in binary on output pins, to save pins: If a system has 8 zones, only 3 pins are needed, while 4 zones need only 2 pins. A decoder can convert the binary encoded zone into the activation of the appropriate zone.

PARTICIPATION  
ACTIVITY

12.9.3: Lawn sprinkler example using a decoder.

Start ☐ 2x speed

Brain

1

0

Sprinkler controller

2x4

i0

i1

y0

y1

y2

y3

0

1

0

0

Zone A

Zone B

Zone C

Zone D

**PARTICIPATION  
ACTIVITY**

12.9.4: Lawn sprinkler system with a decoder.

Consider the example above.

- 1) If the brain outputs 11, what zone is activated?
  - ☐ A
  - ☐ D
- 2) What brain output values will activate all zones at once?
  - ☐ 11
  - ☐ No such values
- 3) If a system has 32 zones instead of 4, how many outputs would the brain need?
  - ☐ 4
  - ☐ 5
  - ☐ 32


### Decoder equation and circuit

A 2x4 decoder has four outputs. Each output's behavior is easily converted to an equation and then to a circuit.

**PARTICIPATION  
ACTIVITY**

12.9.5: Each decoder output is easily converted to an equation and circuit.

Start ☐ 2x speed

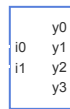

i1	i0	y3	y2	y1	y0	
0	0	0	0	0	1	$y0 = i1'i0'$
0	1	0	0	1	0	$y1 = i1'i0$
1	0	0	1	0	0	$y2 = i1i0'$
1	1	1	0	0	0	$y3 = i1i0$

**PARTICIPATION  
ACTIVITY**

12.9.6: Decoder design.

- 1) How many inputs does a 2x4 decoder have?
 

Check [Show answer](#)
- 2) How many outputs does a 2-input decoder have?
 

Check [Show answer](#)
- 3) How many AND gates does a 2x4 decoder require?
 

Check [Show answer](#)
- 4) How many OR gates does a 2x4 decoder require?
 

Check [Show answer](#)


### Decoder sizes

Other size decoders can be designed similarly.

**PARTICIPATION  
ACTIVITY**

12.9.7: Designing other sized decoders.

Start ☐ 2x speed

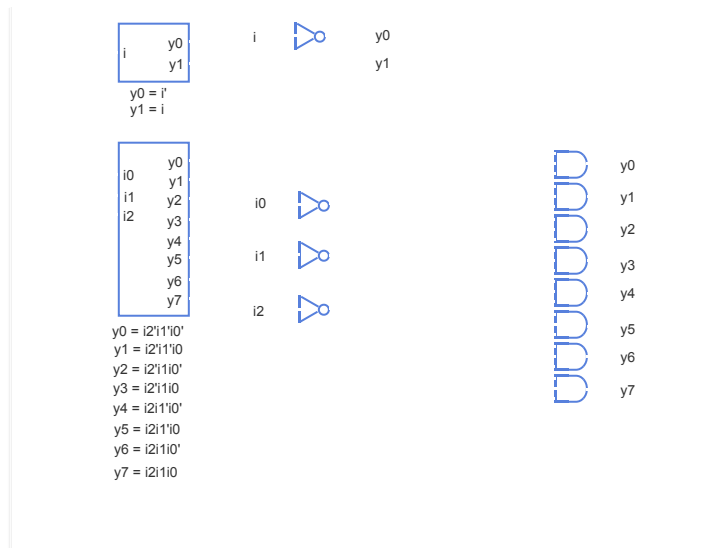

#### PARTICIPATION ACTIVITY 12.9.8: Various sized decoders.

1) How many inputs are required for a decoder with 8 outputs?

Check [Show answer](#)

2) How many inputs are required for a decoder with 2 outputs?

Check [Show answer](#)

3) How many outputs does a 2-input decoder have?

Check [Show answer](#)

4) How many outputs does a 4-input decoder have?

Check [Show answer](#)

5) How many AND gates does a 3x8 decoder require?

Check [Show answer](#)

6) How many OR gates does a 5x32 decoder require?

Check [Show answer](#)

#### Decoder with enable

Some decoders have an additional input called an **enable input** that when 0 sets all outputs to 0s, and when 1 enables the decoder for normal behavior.

A decoder's equations and circuit are easily extended for an enable input by including the enable in each AND.


#### PARTICIPATION ACTIVITY 12.9.9: A decoder with an enable input.

Start ☐ 2x speed



**PARTICIPATION  
ACTIVITY**

12.9.10: Lawn sprinkler example using a decoder.

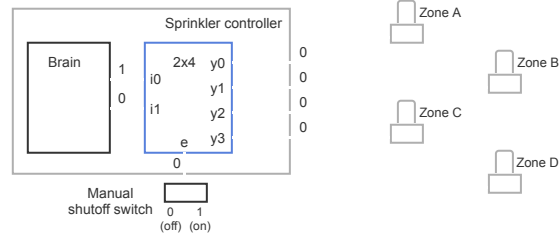Start ☐ 2x speed
**PARTICIPATION  
ACTIVITY**

12.9.11: Decoders with enable.

1) If  $i_1i_0 = 01$  and enable = 1, then  $y_1 =$  \_\_\_\_\_.
Check [Show answer](#)2) If  $i_1i_0 = 00$  and enable = 1, then  $y_1 =$  \_\_\_\_\_.
Check [Show answer](#)3) If  $i_1i_0 = 11$  and enable = 0, then  $y_3 =$  \_\_\_\_\_.
Check [Show answer](#)