

11.9 Sum-of-products form

Sum-of-products

Circuits are commonly designed by creating a simplified expression in sum-of-products form, then converting to a simple circuit.

A **product term** is an ANDing of (one or more) variables, like $ab'c$. A product term is sometimes called just a *product* or just a *term*. An expression in **sum-of-products** form consists solely of an ORing of product terms, like $ab'c + ab$.

Due to similarities with regular algebra, convention uses the word "product" for AND and "sum" for OR; hence the name "sum-of-products". But AND is not really multiplication (product), and OR is not really addition (sum).

PARTICIPATION
ACTIVITY

11.9.1: Products.

Choose Yes if the item is a product term.

1) abc

☐ Yes

☐ No

2) $a'b'cd$

☐ Yes

☐ No

3) $a + bc$

☐ Yes

☐ No

4) a

☐ Yes

☐ No

PARTICIPATION
ACTIVITY

11.9.2: Sum-of-products form.

Choose Yes if the expression is in sum-of-products form.

1) $abc' + abc + ab'c$

☐ Yes

☐ No

2) $abc' + c$

☐ Yes

☐ No

3) $a + c$

☐ Yes

☐ No

4) ab

☐ Yes

☐ No

5) a

☐ Yes

☐ No

6) $a(b + c)$

☐ Yes

☐ No


7) $(a + b)(b' + c)$

☐ Yes

☐ No

Converting sum-of-products to a circuit

 A sum-of-products equation can be easily converted to a circuit, consisting of a column of AND gates (one gate per product term), followed by an OR gate, which is known as a **two-level circuit**. (The NOT gates preceding the AND gates aren't considered a level).



(c) (b) (d) (a)

$$y = fg + e'$$

$$y = efg + e'f$$

$$y = e'f' + ef$$

$$y = f + g$$

Reset

Converting to sum-of-products before creating a circuit

Circuits are commonly created by multiplying out an initial expression into sum-of-products form, then creating a two-level circuit.

PARTICIPATION ACTIVITY

11.9.4: Multiplying out an expression to sum-of-products, before creating a circuit.



Start ☐ 2x speed

Goal: Sound alarm (set output $y = 1$) if alarm is enabled ($e = 1$)
AND (door is open ($d = 1$) OR window is open ($c = 1$)).

$$y = e(d + c)$$

$$y = ed + ec$$



PARTICIPATION ACTIVITY

11.9.5: Multiplying out expressions to convert to sum-of-products form.



Transform to sum-of-products form. Simplify when possible.
Type only the ? part.

1) $y = a(b + b'c)$
 $y = ab + ?$



Check [Show answer](#)

2) $y = c(a + b)$
 $y = ac + ?$



Check [Show answer](#)

3) $y = ab(c + d)$
 $y = abc + ?$



Check [Show answer](#)

4) $y = ac(b + a)$
 $y = abc + ?$



Check [Show answer](#)

5) $y = a + c(b + ab')$
 $y = ? + bc + ab'c$



Check [Show answer](#)

6) $y = a'(b + b'c)$
 $y = a'b + ?$



Check [Show answer](#)

7) $y = (a' + b)(c + d)$
 $y = a'c + a'd + ?$



Example: Interrupt logic component

A processor executes computer programs. Various devices (like keyboards or USB ports) surrounding a processor may request the processor to execute a sub-program on behalf of that device, a request known as an **interrupt**. Devices may be in two categories, low-priority and high-priority, and the processor may disable either category or both.

- Low-priority: keyboard ($k = 1$), mouse ($m = 1$), USB port ($u = 1$). Disable all: $p = 1$.
- High-priority: network interface ($n = 1$), battery backup ($b = 1$). Disable all: $q = 1$.

An interrupt logic component determines whether interrupt requests from devices result in an actual interrupt to the processor ($r = 1$).

PARTICIPATION ACTIVITY 11.9.6: Multiplying out an expression into sum-of-products form before creating a circuit: An interrupt logic example.

Start ☐ 2x speed

Interrupt logic

$$r = (k + m + u)p' + (n + b)q'$$

$$r = kp' + mp' + up' + nq' + bq'$$

PARTICIPATION ACTIVITY 11.9.7: Interrupt logic example.

Consider the above interrupt logic example.

- 1) How many inputs does the interrupt logic component have?

 Check [Show answer](#)
- 2) How many outputs does the interrupt logic component have?

 Check [Show answer](#)
- 3) Did the designer originally capture the interrupt logic's behavior as a sum-of-products equation? Type yes or no.

 Check [Show answer](#)
- 4) How many product terms are in the sum-of-products form of the interrupt logic's equation?

 Check [Show answer](#)
- 5) How many AND gates are in the interrupt logic's circuit?

 Check [Show answer](#)