

11.1 Electronics and digital systems

Voltage and current

Electrical systems are ubiquitous, in appliances, computers, cars, etc. An **electrical system** involves movement of charged electrons through wires.

- **Voltage** is the potential for charge to move. Voltage is measured in **Volts**.
- **Current** is the amount of charge flow. Current is measured in **Amps**.
- **Resistance** is a wire's opposition to flow. Resistance is measured in **Ohms**.

An example electrical system is a lamp that passes current through a glowing resistor in a light bulb. The more current, the brighter the glow.

PARTICIPATION
ACTIVITY

11.1.1: Voltage and current.

Start ☐ 2x speed

6 V

▼

○

▼

0 V

Above, the zigzag line represents a resistor.

Voltage is like the water pressure in a faucet for a garden hose. Current is like the amount of water actually flowing through the hose. Resistance is like a thin hose more-strongly resisting flow than a thick hose.

Current flows from a higher-voltage point to a lower-voltage point on a wire. 0 V is commonly called **ground** and drawn as three line segments, as above.

Voltage (V), current (I), and resistance (R) are related as $V = IR$, called **Ohm's Law**.

PARTICIPATION
ACTIVITY

11.1.2: Terminology: Electrical systems.

Ohms Voltage $V = IR$ Volts Resistance Current Amps

Potential for charge to move

Amount of charge flow

Opposition to flow

Units of voltage

Units of current

Units of resistance

Ohm's Law

Reset

PARTICIPATION
ACTIVITY

11.1.3: Voltage, current, and resistance.

1) Increasing voltage does what to current?

☐ Increases

☐ Decreases

☐ Doesn't change

2) Decreasing resistance does what to current.

☐ Increases

☐ Decreases

☐ Doesn't change

3) If V is 6 V and R is 2 Ohms, I = ?

☐ 12

☐ 6
☐ 3

4) If V is 6 V and R is 1 Ohm, $I = ?$

☐ 12
☐ 6
☐ 3

5) If V is 6 V and R is 0 Ohms, $I = ?$

☐ 6
☐ 3
☐ Infinity

6) If V is 6 V and R is infinite, $I = ?$

☐ 0
☐ 3
☐ Infinity

The voltage on a wire with no resistance is the same everywhere on the wire. But voltage drops across a resistor as $V = IR$.

PARTICIPATION ACTIVITY
11.1.4: $V = IR$.

1) What is the current I ?
 A
 Check [Show answer](#)

2) What is the voltage at X?
 V
 Check [Show answer](#)

3) What is the voltage at Y?
 V
 Check [Show answer](#)

4) What is the voltage at Z?
 V
 Check [Show answer](#)

Note: Nearly every wire has some tiny resistance (with the exception of superconductors), but that resistance is commonly ignored.

Note: Convention is to show current flowing from higher voltage to lower voltage, even though actual flow is in the other direction, due to electrons having negative charge. But the net effect is the same.

Switches

A **switch** is an electronic device that acts like a wire (a.k.a. "conducts") between two terminals if the switch is configured to on. A light-switch is an example.

PARTICIPATION ACTIVITY
11.1.5: Switches can be configured to conduct.

Start ☐ 2x speed

5 V

0 V

An **electronically-controlled switch** has another input terminal whose voltage can turn the switch on. The terminal that controls an electronically-controlled switch is known as the **control input**.

**PARTICIPATION
ACTIVITY**

11.1.6: An electronically-controlled switch is controlled by a control input.

Start ☐ 2x speed

5 V




0 V



0 V

Figure 11.1.1: Switches: Relay, vacuum tube, discrete transistor, and integrated circuit (having millions of switches inside).

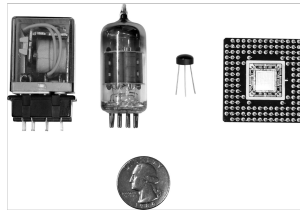

Switches in the early 1900s were large, each being several inches long. A **transistor** is a smaller simpler switch with no mechanical parts, invented in 1947.

**PARTICIPATION
ACTIVITY**

11.1.7: Switches.

1) A basic ____ either conducts or doesn't.

Check [Show answer](#)

2) An ____-controlled switch has another input whose voltage turns the switch on or off.

Check [Show answer](#)

3) A ____ is a small switch with no mechanical parts.

Check [Show answer](#)

CMOS transistors

A **CMOS transistor** is a popular transistor type. Two types of CMOS transistors are pMOS and nMOS. An **nMOS** transistor conducts when its control input is 1. A **pMOS** transistor conducts when its control input is 0.

**PARTICIPATION
ACTIVITY**

11.1.8: CMOS transistors.

Start ☐ 2x speed

nMOS

pMOS

1

0 ○


Conducts when 1

Conducts when 0

PARTICIPATION ACTIVITY 11.1.9: pMOS and nMOS transistors.

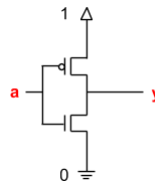- 1) Does a pMOS conduct if the control input is 0?
☐ Yes
☐ No
- 2) Does an nMOS conduct if the control input is 0?
☐ Yes
☐ No
- 3) Does a pMOS conduct if the control input is 1?
☐ Yes
☐ No
- 4) Does an nMOS conduct if the control input is 1?
☐ Yes
☐ No

PARTICIPATION ACTIVITY 11.1.10: A simple circuit of pMOS and nMOS transistors.



- 1) What is y when a is 0?
☐ 1
☐ 0
- 2) What is y when a is 1?
☐ 1
☐ 0

Digital systems


A **circuit** is a path through which electrical current can flow. In a circuit of switches, some wires have a high voltage, some have low voltage. High is labeled 1, low 0. (High is usually not 1 V; high could be 1.3 V, for example). A **digital circuit** has voltages that are treated as either high or low, and is typically built as a connection of switches. In contrast, an **analog system** has voltages that are treated as having infinite values like 0.15, 0.2, 0.333, etc. Digital circuits form the basis of useful systems like smartphones, computers, medical devices, and more.

The word "system" means a set of connected things forming a complex whole. Thus, digital circuits are often referred to more generally as **digital systems**

This material focuses on **digital design**. Creating digital circuits to achieve desired digital system behavior that converts digital inputs into desired digital outputs.


PARTICIPATION ACTIVITY 11.1.11: Digital systems.

Start ☐ 2x speed

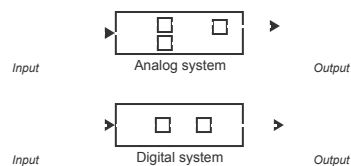

Why the name 'digital'?

The term "digit" literally means finger (or toe) ([see Oxford dictionary definition](#)). Because people have a finite number of fingers, and digital circuits have a finite number of voltages (usually just two: high and low), the term "digital" is used. (Digit is also used to refer to a place in a number, such as 97 having two digits; that use of digit stems from people counting with their fingers).

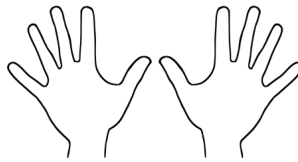

**PARTICIPATION
ACTIVITY**

11.1.12: Digital circuits.



- 1) A ____ is path through which electrical current can flow.

Check [Show answer](#)



- 2) An ____ system's voltages can assume infinite values.

Check [Show answer](#)



- 3) A ____ system's values can assume just two values, labeled 1 and 0.

Check [Show answer](#)



Exploring further:

- [Transistor \(Wikipedia\)](#)
- [CMOS \(Wikipedia\)](#)

 [Provide feedback on this section](#)