

11.6 Equations to/from circuits

Equations to circuits


An equation is one way to represent a Boolean function. Another way is using a circuit.

An equation can be converted to a circuit by converting each operation to a gate. Conversion is done first for items within parentheses. In a term like cd' , NOT is converted before AND or OR. Converting behavior (like an equation) to a circuit is called **design**.


PARTICIPATION ACTIVITY 11.6.1: Convert equation to circuit.

Start ☐ 2x speed

$w = (a + b)cd'$

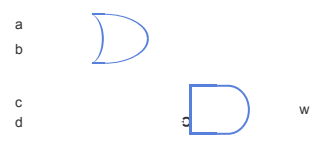

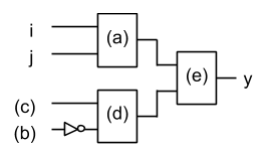PARTICIPATION ACTIVITY 11.6.2: Converting an equation to a circuit.



Use the figure above to determine the missing value.
Original equation: $y = ij + mn'$

1) (a)

- ☐ AND
- ☐ OR
- ☐ NOT

2) (b)

- ☐ m
- ☐ n
- ☐ mn'
- ☐ i

3) (c)

- ☐ m
- ☐ n
- ☐ mn'
- ☐ i

4) (d)

- ☐ AND
- ☐ OR
- ☐ NOT

5) (e)

- ☐ AND
- ☐ OR
- ☐ NOT

Example: Airbag enabler


Figure 11.6.1: Airbags deployed.



Cars have airbags that deploy during an accident to reduce injuries to occupants. Airbags can harm kids, and aren't needed for non-human objects. Thus, cars have sensors to help detect whether an airbag should be enabled by a large enough human being seated. In one car, a seat back sensor detects a heartbeat ($h = 1$). A seat bottom sensor indicates if over 60 pounds is detected ($w = 1$). A switch can be used to manually disable the airbags ($d = 1$). An output e indicates that the airbag is enabled ($e = 1$).

A designer specifies the system as: $e = hwd'$ (heartbeat detected, and enabled if weight over 60, and not manually disabled).

Figure 11.6.2: Airbag enabler system.

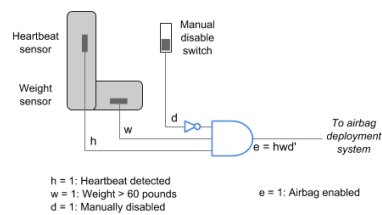

**PARTICIPATION
ACTIVITY**

11.6.3: Airbag example.

- 1) What is h if a heartbeat is detected?

Check [Show answer](#)

- 2) What is w if the sensed weight is 30 pounds?

Check [Show answer](#)

- 3) What is e if $h = 1$, $w = 1$, and $d = 1$?

Check [Show answer](#)

- 4) e becomes an input to another system, the airbag deployment system. That system has another input to detect a hard front-end collision ($c = 1$). That system's output a should be 1 if a hard collision is detected and the airbag is enabled. Write the equation for a .

Check [Show answer](#)

- 5) Write an equation to deploy the airbag ($a = 1$) only if a collision is detected ($c = 1$) and the airbag is enabled. Use input variables h , w , d , c only (do not use e). Order input variables alphabetically. Do not use parentheses.

Check [Show answer](#)

- 6) A light illuminates if the airbag is disabled. Which is the appropriate equation to turn on the light ($o = 1$)?

$o = h'w'd$

$o = (hwd)'$



(Note: Answer by re-typing one of the equations provided)

Check

Show answer

Example: Aircraft lavatory sign

Airplanes typically have a lighted sign to let passengers know if at least one of several lavatories (bathrooms) is available, so that passengers can choose to stay seated until a bathroom becomes available. A designer may think about the logic as follows: If all doors are locked, the sign should be off, otherwise the sign should be on. From that thought, the designer may create an equation.

PARTICIPATION ACTIVITY 11.6.4: Aircraft lavatory sign.

Start ☐ 2x speed

Lavatory available

y 1

Logic

$y = (abc)'$

a 1 b 1 c 0

Lavatory door Lavatory door Lavatory door

Locked signals

PARTICIPATION ACTIVITY 11.6.5: Lavatory sign example.

1) If a, b, c are all 1's, should the sign illuminate?

☐ Yes

☐ No

2) The designer created the equation $y = (abc)'$, and then a circuit consisting of AND followed by ____

☐ NOT

☐ OR

Circuits to equations

A circuit can be converted to an equation. Starting from the inputs, the process replaces gates by terms while moving towards the output, labeling gate outputs along the way. Converting a circuit to behavior (like an equation) is called **analysis**.

PARTICIPATION ACTIVITY 11.6.6: Circuit to equation.

Start ☐ 2x speed

a b

c d

(ab)

(c'd)

(ab) + (c'd)

y

$y = (ab) + (c'd)$

A circuit whose output value is determined solely by the present *combination* of input values is called a **combinational circuit**. A combinational circuit is also called **combinational logic**.

A circuit whose output values may depend on the past *sequence* of input values, and not just the present input values, is called a **sequential circuit**. This material discusses sequential circuits later.

PARTICIPATION ACTIVITY 11.6.7: Combinational vs. sequential circuits.

Indicate whether each description would involve a combinational or sequential circuit.

1) If one or more people are in a room, turn on the lights.

- ☐ Combinational
- ☐ Sequential

2) If the weight in an elevator exceeds 1500 pounds, sound an alarm.

- ☐ Combinational
- ☐ Sequential

3) If the sleep mode button is pressed and released, turn phone ringer off until the sleep mode button is pressed again.

- ☐ Combinational
- ☐ Sequential

4) Turn faucet on while motion is detected.

- ☐ Combinational
- ☐ Sequential

5) If the garage door button is pressed, turn motor on until garage door is fully opened.

- ☐ Combinational
- ☐ Sequential

CHALLENGE ACTIVITY

11.6.1: Convert the equation to a circuit.

Convert the equation provided to a circuit.

- Add gate to workspace: Click the gate image in the bottom-right.
- Create wire: Drag from a pin.
- Toggle input between 0 and 1: Click on input.
- Delete gate or wire: Select item then click "Delete selected item(s)".

Start



Check

Next

[Provide feedback on this section](#)